

Arbeitskreis Hardware

Prof. Dr. Michael Rohs, Dipl.-Inform. Sven Kratz

michael.rohs@ifi.lmu.de


MHCI Lab, LMU München

Schedule (preliminary)

Date	Topic (preliminary)
2.5.	Introduction to embedded interaction, microcontrollers, hardware & software tools
9.5.	<i>keine Veranstaltung (CHI)</i>
16.5.	soldering ISP adapter, AVR architecture
23.5.	LED displays, LED multiplexing, transistors, electronics basics
30.5.	AVR architecture, AVR assembler, sensors: light, force, capacity, acceleration, etc.
6.6.	PCB design & fabrication, EAGLE, 3D printing
13.6.	<i>keine Veranstaltung (Pfingsten)</i>
20.6.	I2C: interfacing to other chips (EEPROM, real-time clock, digital sensors)
27.6.	Displays (character LCDs, graphics LCDs), audio (speakers, amplification, op-amps)
4.7.	Actuation: stepper motors, servo motors
11.7.	Communication: fixed-frequency RF, ZigBee, Bluetooth
18.7.	Project
25.7.	Project

LEDs

- Quickly switchable, power-efficient light sources
 - different types covering different parts of the visible spectrum (and beyond: IR LEDs, UV LEDs)
- Anode (long lead) goes to positive potential
- Cathode (short lead) goes to negative potential
- LEDs operate like voltage-controlled switches
 - little current below turn-on voltage (silicon: 0.7V)
 - very high current above → LEDs need current-limiting resistors
- LEDs are diodes: no current in reverse direction
- Typical forward current: 20mA, typical forward voltage 2V

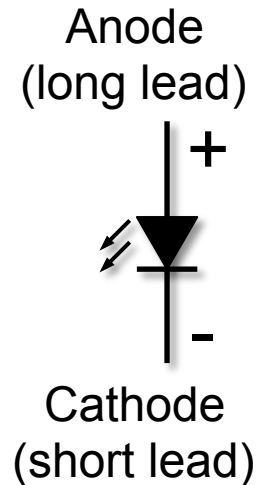


LEDs

- Intensity of light proportional to current
 - can also use PWM to control brightness
 - light covers narrow spectrum only, except for white LEDs
- Forward voltage drop depends on color, e.g.:

Color	Fwd. current	Fwd. voltage
red	20mA	2.0V
green	20mA	3.5V
blue	20mA	3.7V
white	20mA	3.5V

- Can go up to 100mA (peak current)



LED light spectra

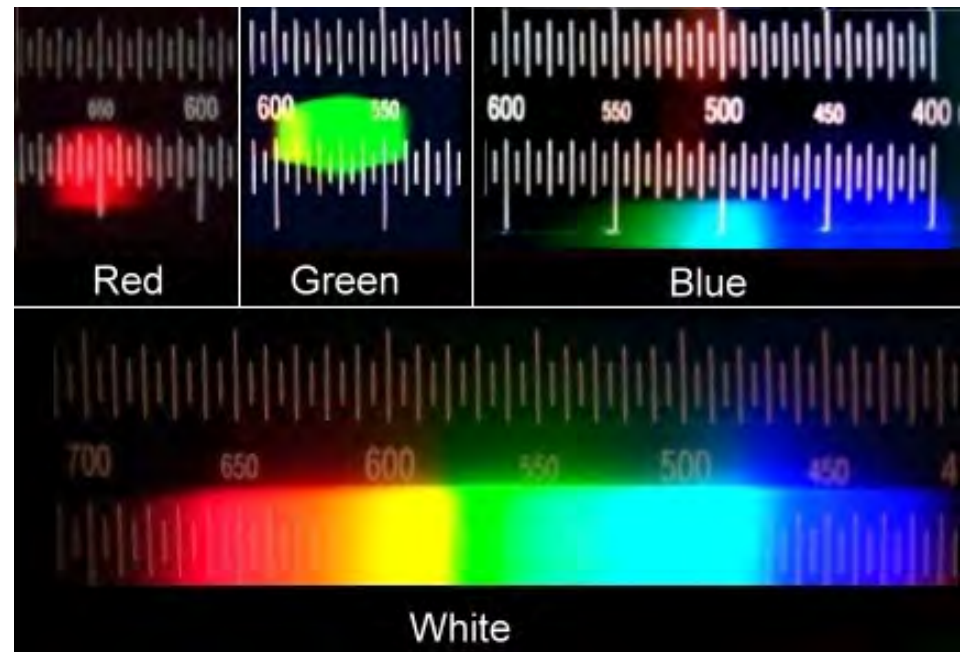

© Anton (rp), BY-CC-SA

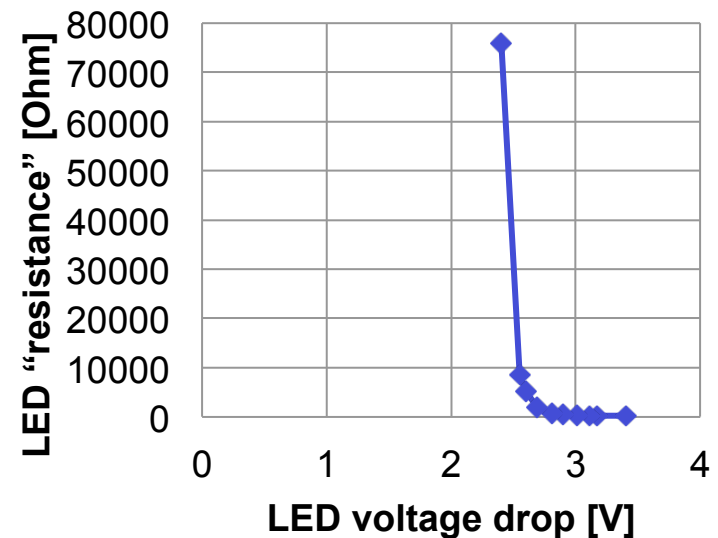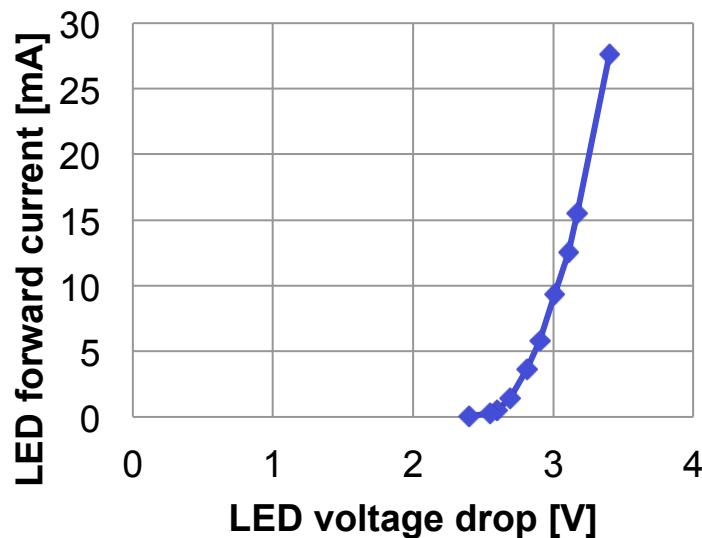Example: Blue LED Voltage Drop

- $U_f = 3.2V$, $I_f = 20mA$
- Current limiting resistor: $U_R = U - U_f = 5 - 3.2 = 1.8V$
 $R = U_R / I = 1.8V / 0.020A = 90\Omega$



$$R_f = U_f / I$$

LED Brightness Experiment

- Assume LED brightness is proportional to current
- Is PWM duty cycle proportional to brightness? Hypothesis?
- For increasing values of PWM duty cycle value d
 - Set d for LED₁
 - Control current through LED₂ to match brightness of LED₁
 - Match brightness with potentiometer
 - Measure current
- Draw curve
 - x-axis = current
 - y-axis = matching PWM duty cycle value
- Check whether duty cycle is proportional to current (and thus brightness)

RGB LEDs


- Red, green, and blue in one package
- Different forward voltages ($I_f = 20\text{mA}$):

- $U_{f,\text{red}} = 2.0\text{V}$

- $U_{f,\text{green}} = 2.2\text{V}$


- $U_{f,\text{blue}} = 3.8\text{V}$

- Example (right): 30° angle, 2x blue

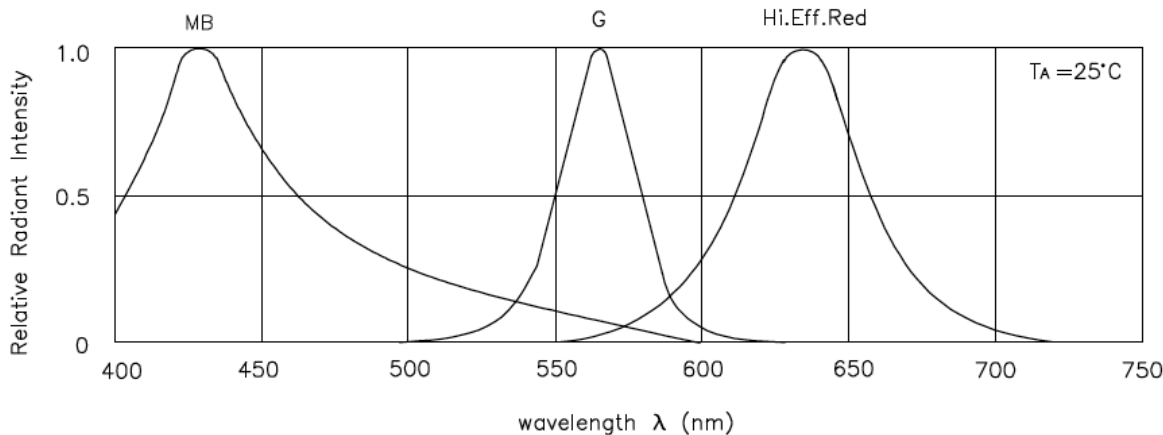

RELATIVE INTENSITY Vs. WAVELENGTH

Source: Kingbright Datasheet



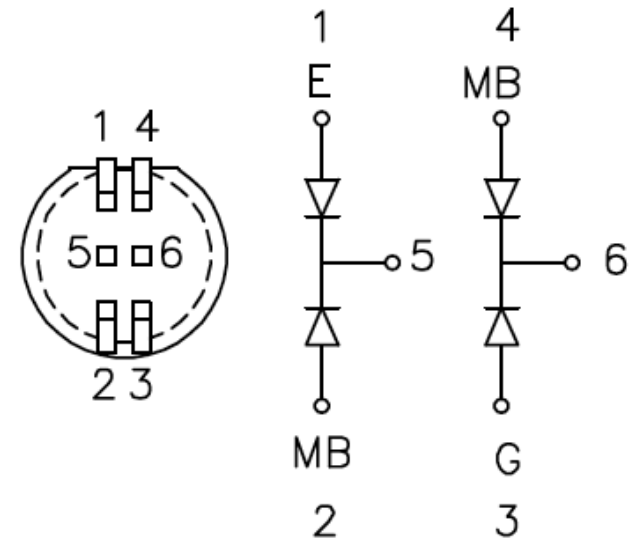


Source: Kingbright Datasheet

LED Displays: 7-Segment, 10-Bar



- 7-segment display (green)

- $U_f = 2.2V, I_f = 20mA$

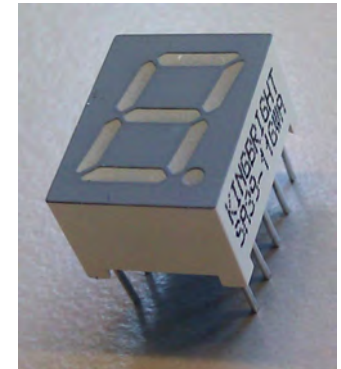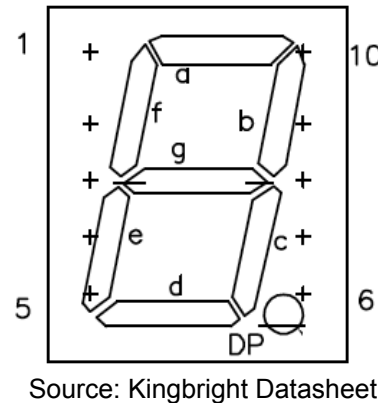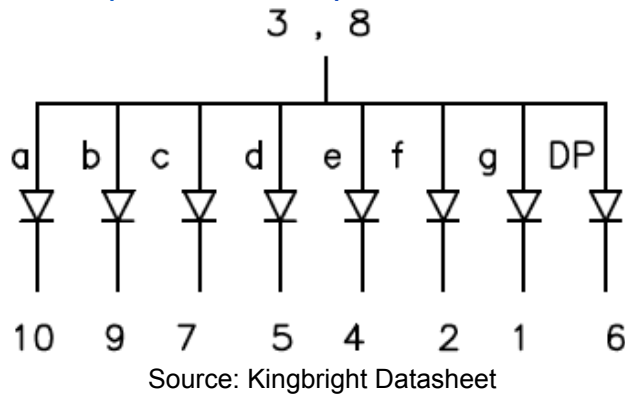


- 10-bar display (red)

- $U_f = 2.0V, I_f = 20mA$

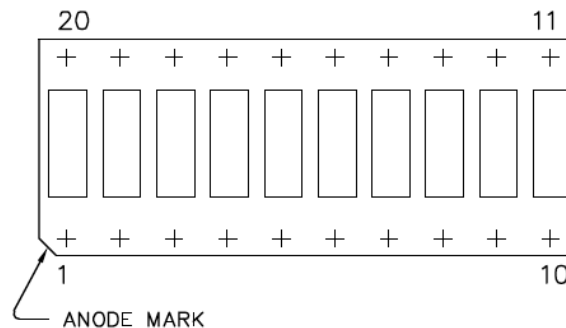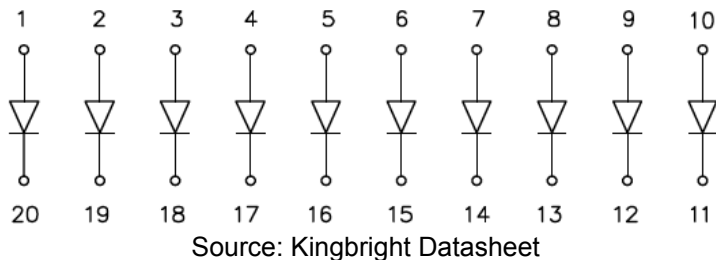



LED Displays: 5x7-Matrix

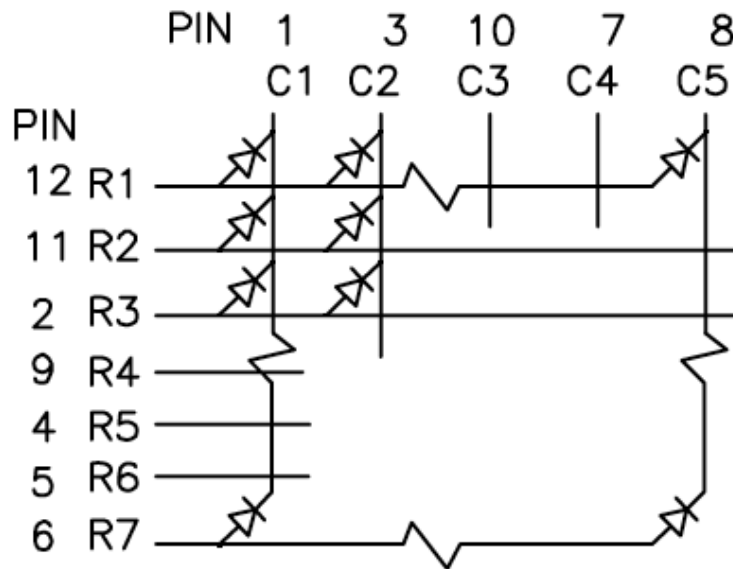- 5x7 dot matrix display (red)
 - $U_f = 2.25V$, $I_f = 20mA$



Source: Kingbright Datasheet

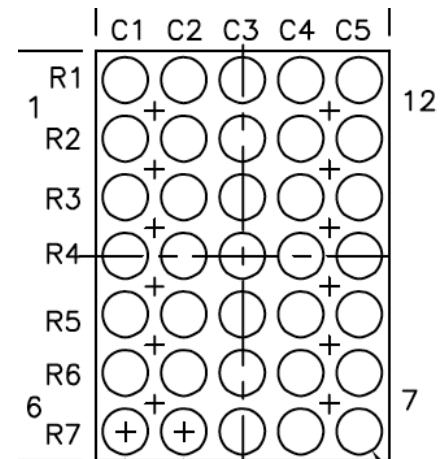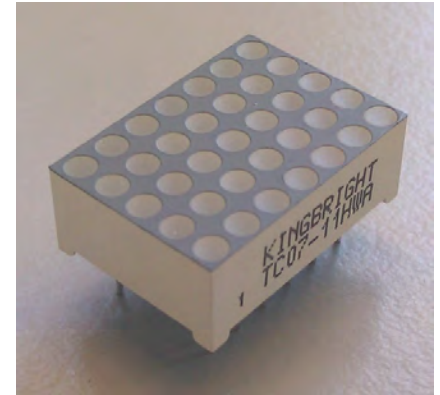
- Check total power consumption
 - ATtiny can only drive up to 40mA per pin
 - use transistor if necessary



Source: Kingbright Datasheet

More LEDs than μC Pins

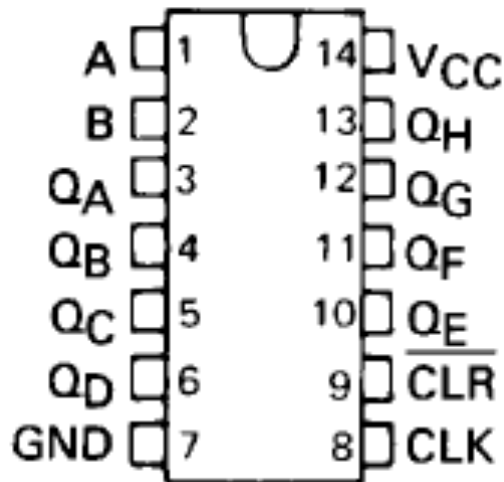- 8-bit serial-in, parallel-out shift register 74LS164N



Source: TI Datasheet


FUNCTION TABLE

INPUTS				OUTPUTS		
$\overline{\text{CLEAR}}$	CLOCK	A	B	Q_A	$Q_B \dots$	Q_H
L	X	X	X	L	L	L
H	L	X	X	Q_{A0}	Q_{B0}	Q_{H0}
H	\uparrow	H	H	H	Q_{An}	Q_{Gn}
H	\uparrow	L	X	L	Q_{An}	Q_{Gn}
H	\uparrow	X	L	L	Q_{An}	Q_{Gn}

Source: TI Datasheet

- $Q_A = A$ and B , unused input must be H
- CLK: low-to-high shifts data one place right
- maximum clock frequency: 25 MHz
- $V_{cc} = 5\text{V}$, $I_{cc} = 16\text{mA}$
- $I_{OS} = -10..-27.5\text{mA}$ (short-circuit output current)

Driving more LEDs with a transistor

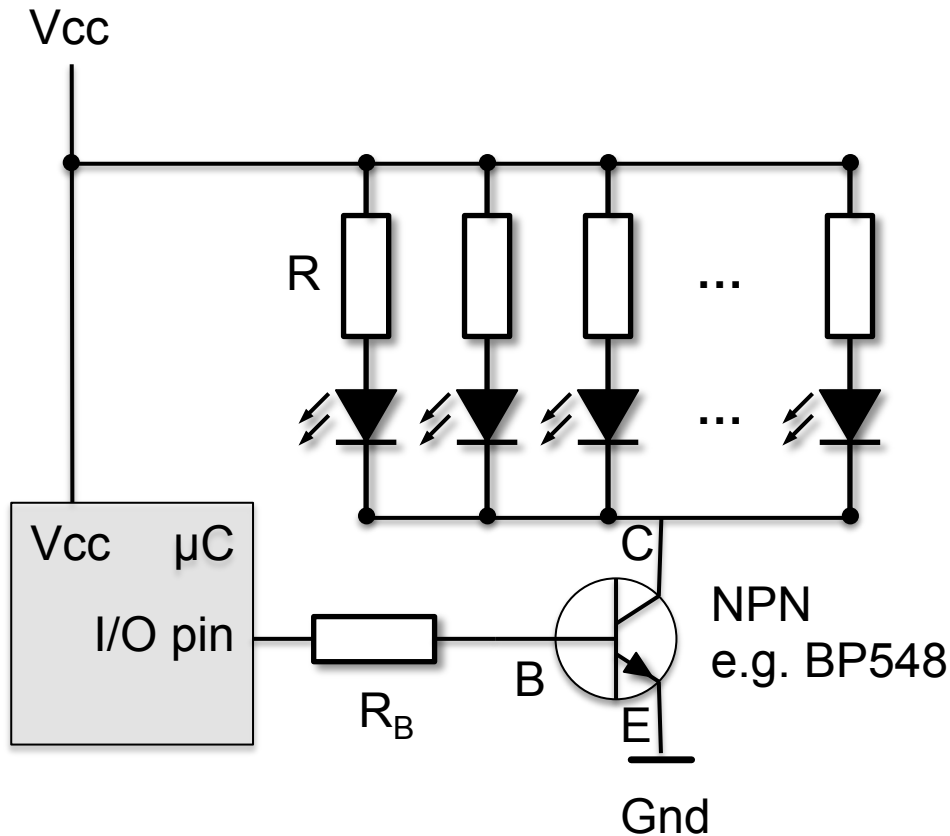

- Given
 - $V_{CC} = 5V$
 - red LEDs: $U_F = 2V$, $I_F = 20mA$
 - BC548A: $I_{C,max} = 100mA$,
current gain $\beta = h_{FE} = 110..220$

- Drive 5 LEDs: 100mA

$$h_{FE} = 120 \text{ (@ } I_C = 100mA, V_{CE} = 5V)$$

$$V_{CE(sat)} = 0.2V \text{ (@ } I_C = 100mA, V_{CE} = 5V)$$

$$V_{BE(sat)} = 0.7V \text{ (@ } I_C = 100mA, V_{CE} = 5V)$$

- R? R_B ?


$$U_R = V_{CC} - V_{CE(sat)} - V_F$$

$$R = U_R / I_F$$


$$I_C = h_{FE} I_B$$

Behavior of Transistors (active region)

NPN (e.g. BC548)

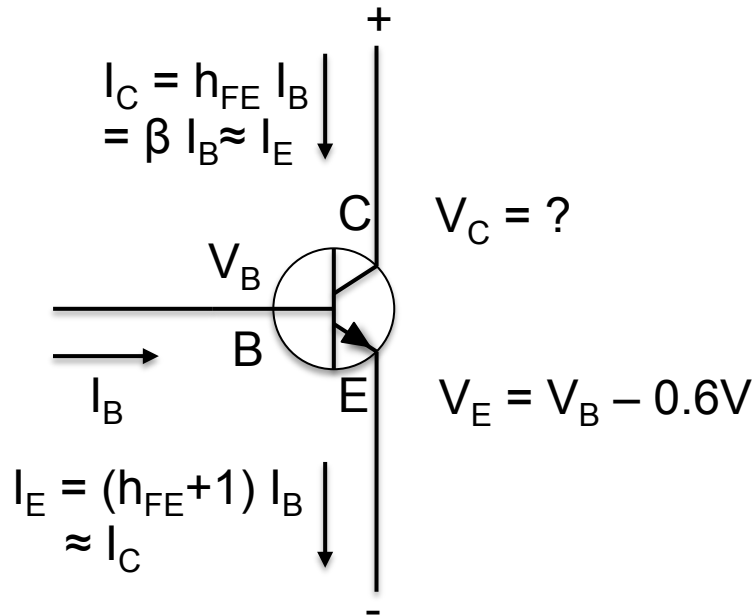

PNP (e.g. BC558)

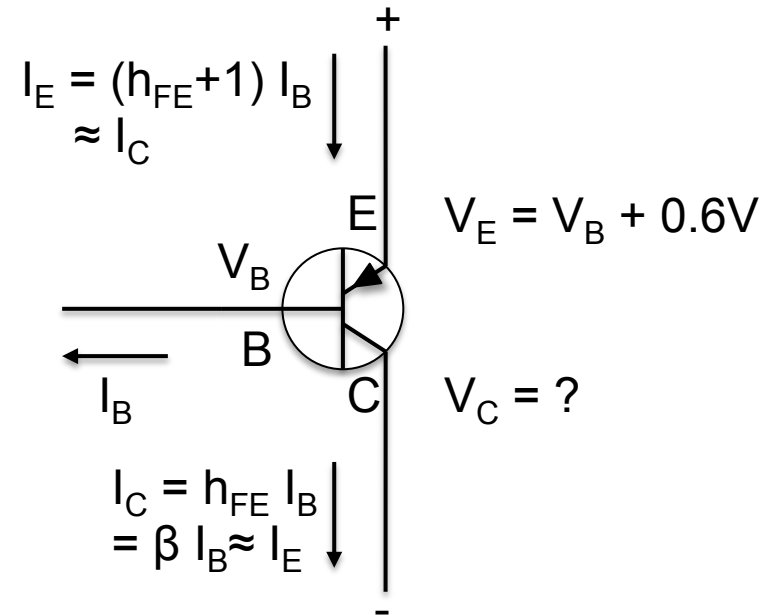

- $I_C = h_{FE} I_B = \beta I_B$
- $I_E = I_C + I_B$
- $I_E \approx I_C$

Typical Characteristics of BC548

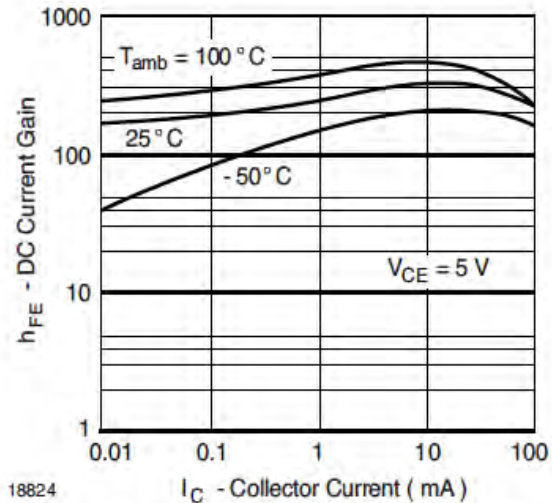


Figure 2. DC Current Gain vs. Collector Current

Source: Vishay Datasheet


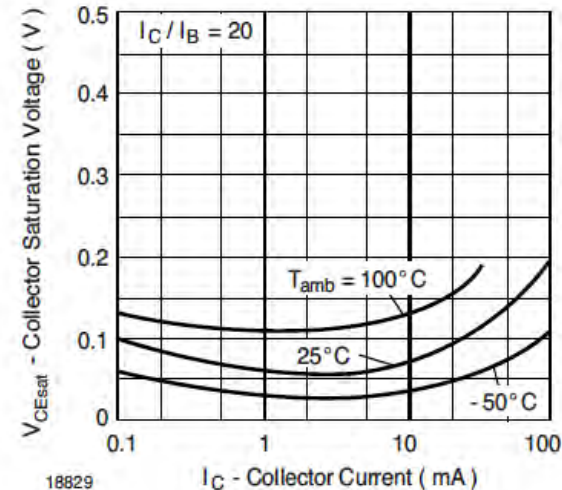


Figure 7. Collector Saturation Voltage vs. Collector Current

Source: Vishay Datasheet

- $I_C = h_{FE} I_B = \beta I_B$
- $I_E = I_C + I_B$
- $I_E \approx I_C$

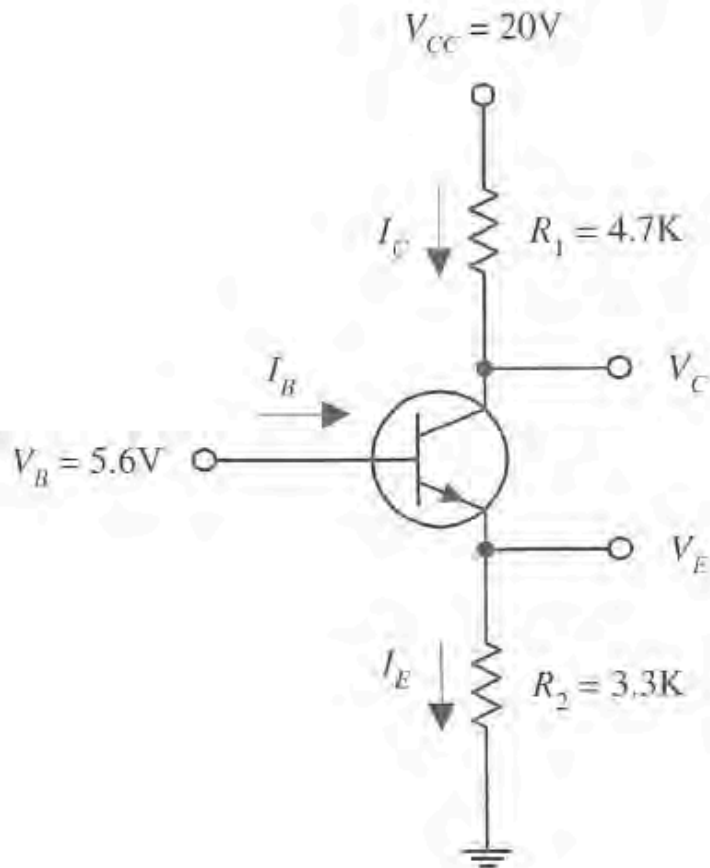EXAMPLE 1 Given $V_{CC} = +20\text{ V}$, $V_B = 5.6\text{ V}$, $R_1 = 4.7\text{ k}\Omega$, $R_2 = 3.3\text{ k}\Omega$, and $h_{FE} = 100$, find V_E , I_E , I_B , I_C , and V_C .



$$V_E = V_B - 0.6\text{ V}$$

$$V_E = 5.6\text{ V} - 0.6\text{ V} = 5.0\text{ V}$$

$$I_E = \frac{V_E - 0\text{ V}}{R_2} = \frac{5.0\text{ V}}{3300\ \Omega} = 1.5\text{ mA}$$

$$I_B = \frac{I_E}{(1 + h_{FE})} = \frac{1.5\text{ mA}}{(1 + 100)} = 0.015\text{ mA}$$

$$I_C = I_E - I_B \approx I_E = 1.5\text{ mA}$$


$$V_C = V_{CC} - I_C R_1$$

$$V_C = 20\text{ V} - (1.5\text{ mA})(4700\ \Omega)$$

$$V_C = 13\text{ V}$$

Source: Paul Scherz: Practical Electronics for Inventors. 2nd edition, McGraw-Hill, 2007.

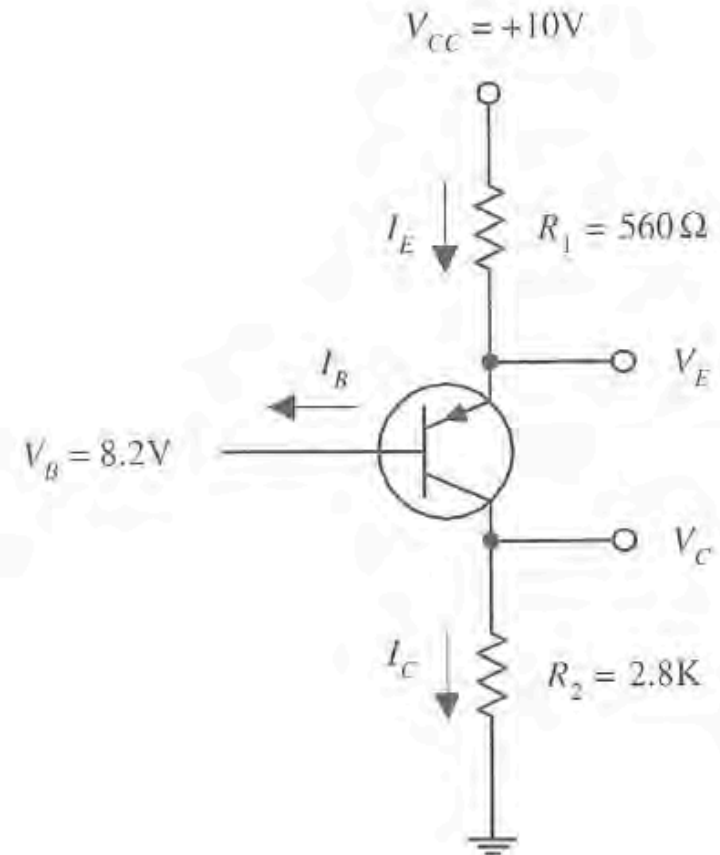EXAMPLE 2 Given $V_{CC} = +10\text{ V}$, $V_B = 8.2\text{ V}$, $R_1 = 560\ \Omega$, $R_2 = 2.8\text{ k}\Omega$, and $h_{FE} = 100$, find V_E , I_E , I_B , I_C , and V_C .



$$V_E = V_B + 0.6\text{ V}$$

$$V_E = 8.2\text{ V} + 0.6\text{ V} = 8.8\text{ V}$$

$$I_E = \frac{V_{CC} - V_E}{R_1} = \frac{10\text{ V} - 8.8\text{ V}}{560\ \Omega} = 2.1\text{ mA}$$

$$I_B = \frac{I_E}{(1 + h_{FE})} = \frac{2.1\text{ mA}}{(1 + 100)} = 0.02\text{ mA}$$

$$I_C = I_E - I_B \approx I_E = 2.1\text{ mA}$$

$$V_C = 0\text{ V} + I_C R_2$$



$$V_C = 0\text{ V} + (2.1\text{ mA})(2800\ \Omega)$$

$$V_C = 5.9\text{ V}$$


Source: Paul Scherz: Practical Electronics for Inventors. 2nd edition, McGraw-Hill, 2007.

Transistors

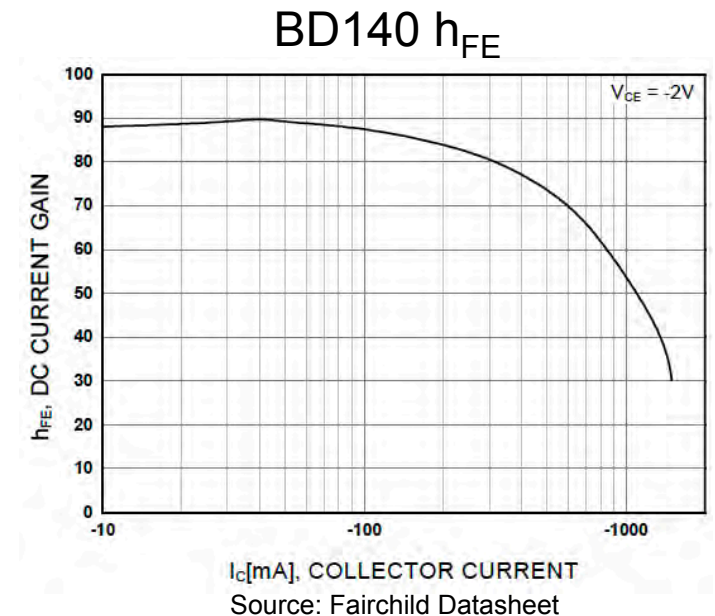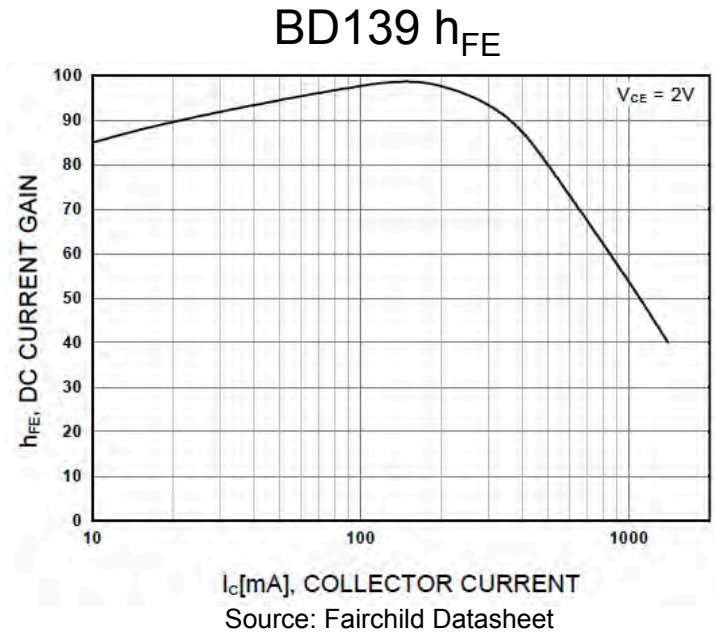- BD139 – NPN
 - maximum ratings:
 $I_C = 1.5A$, $I_B = 0.5A$
 - $V_{CE(sat)} = 0.5V$, $V_{BE} = 1V$
 - $h_{FE} = 63..160 @ I_C = 150mA$, $V_{CE} = 2V$
- BD140 – PNP
 - maximum ratings:
 $I_C = -1.5A$, $I_B = -0.5A$
 - $V_{CE(sat)} = -0.5V$, $V_{BE} = -1V$
 - $h_{FE} = 40..250 @ I_C = -150mA$, $V_{CE} = -2V$




Multiplexing LEDs

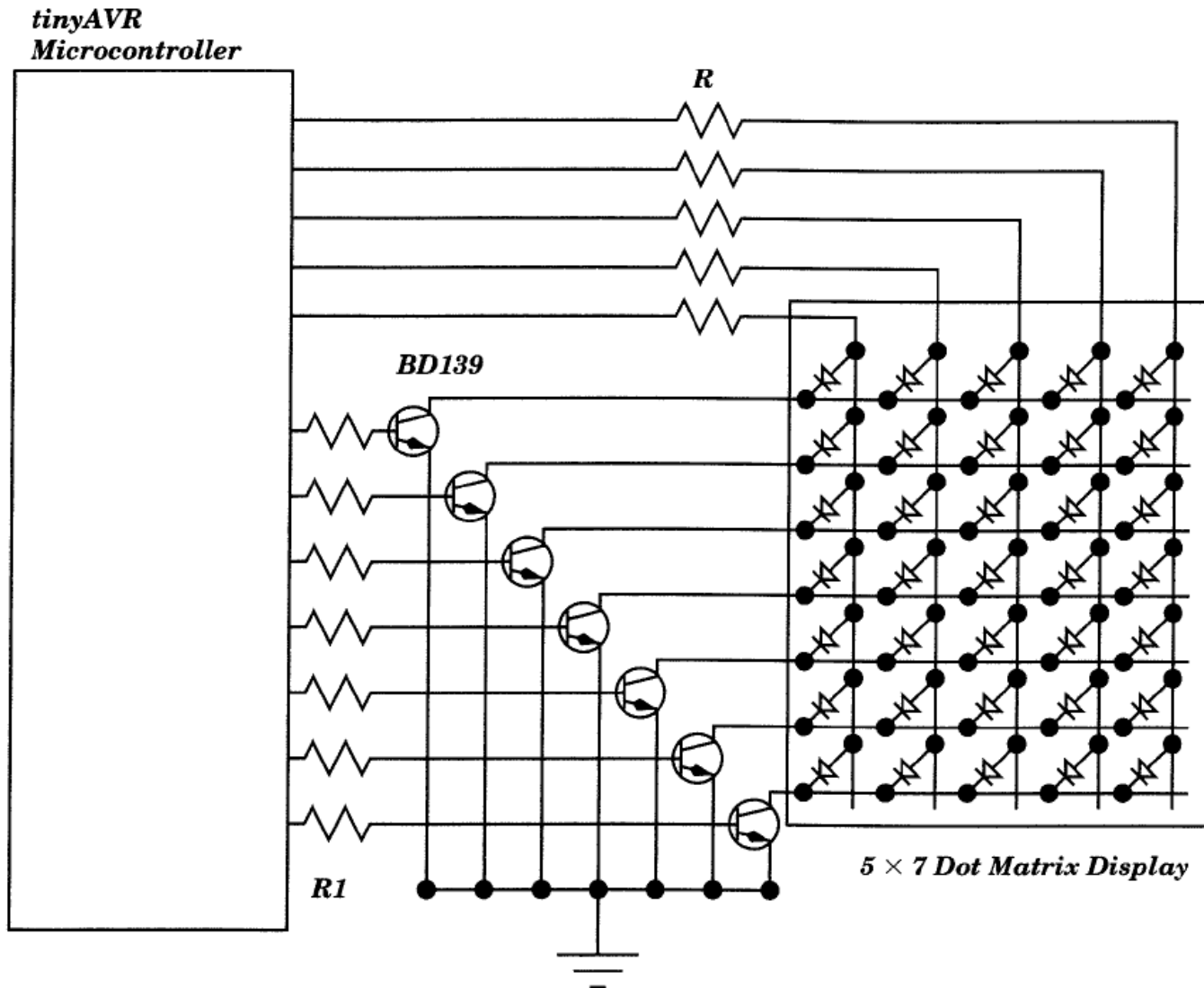


Source: Gadre, Malhotra: tinyAVR Microcontroller Projects for the Evil Geniuses. McGraw-Hill, 2011.

Multiplexing LEDs

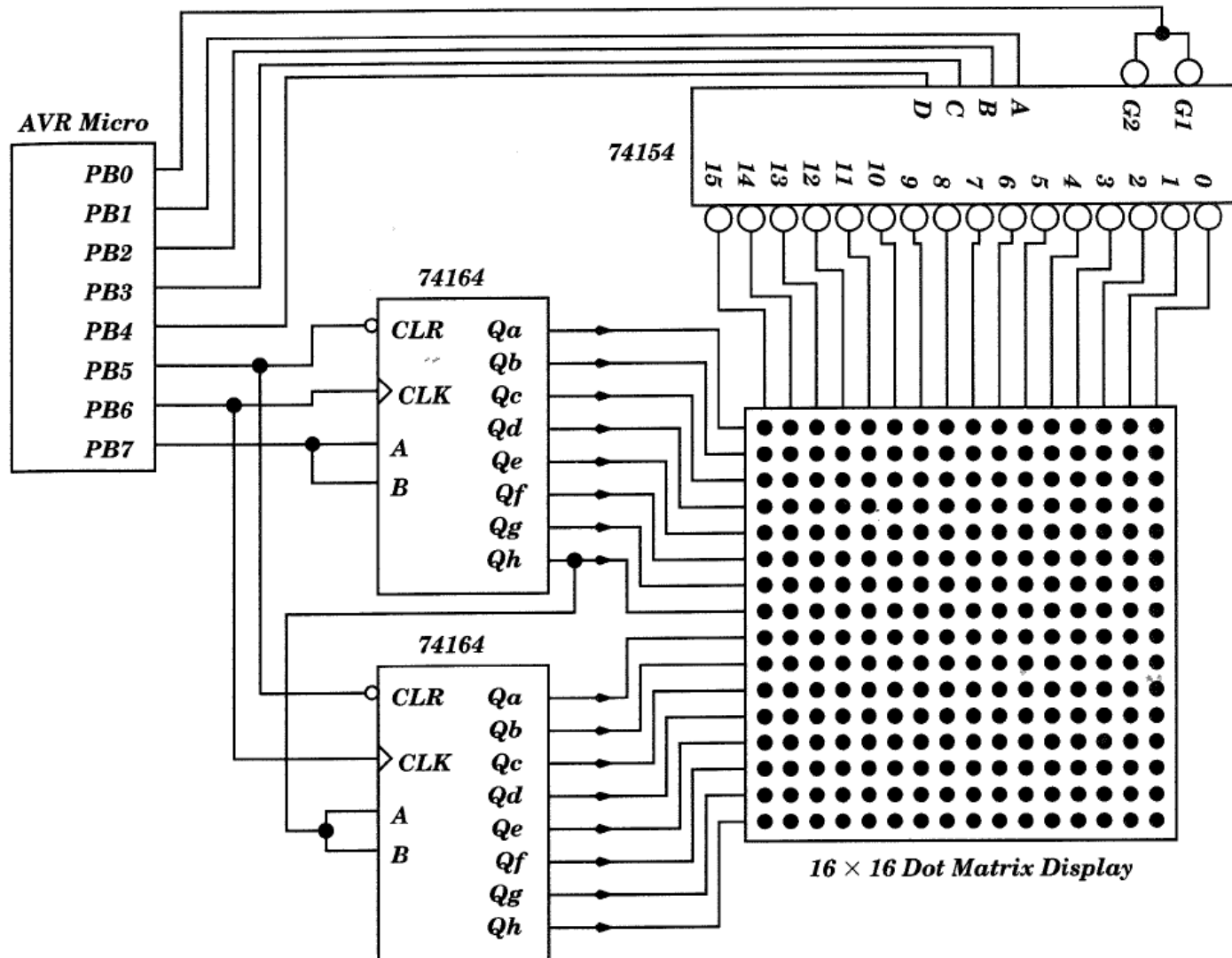

Source: Gadre, Malhotra: tinyAVR Microcontroller Projects for the Evil Geniuses. McGraw-Hill, 2011.

Charlieplexing LEDs

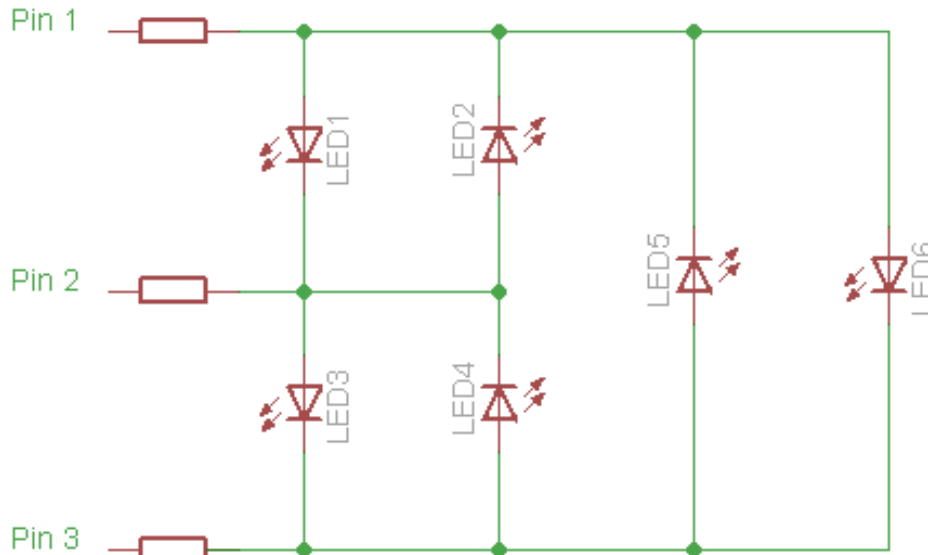

Source: Wikipedia, Author: Dan Kouba, public domain

LED	Pin1	Pin2	Pin3
D1	1	0	Z
D3	Z	1	0
D6	1	Z	0
D4	Z	0	1
D2	0	1	Z
D5	0	Z	1

- Enables one LED at a time
 - N LEDs, each only on $1/N^{\text{th}}$ of the time
- Z = tri-state (high impedance state, “no” current)

Exercise: Controlling LEDs

- Control brightness of two LEDs with PWM
 - Attach 2 LEDs to an ATtiny13
 - Periodically
 - Over 2s: increase brightness of LED₁ from dark to maximum, decrease brightness LED₂ from maximum to dark
 - Over 2s: increase brightness of LED₂ from dark to maximum, decrease brightness LED₁ from maximum to dark
 - Over 2s: no change in LED brightness
 - Use timers and interrupts as needed
- Control brightness of an LED using PWM and two buttons
 - Attach LED to an ATtiny13
 - While button₁ is pressed, slowly increase brightness
 - While button₂ is pressed, slowly decrease brightness

Button De-Bouncing

- Activate pull-up resistor on pin
 - Pull-up puts pin into defined state
 - (see previous slides on pin configurations)
- Connect button to GND
 - Pin will be high until button pressed
- De-Bouncing
 - Button contacts bounce, which generates many spikes
 - Hardware solutions: SR latch, capacitor
 - Software solution:
 - wait for 10-20ms after first event




Source: Wikipedia, Author: Tomoldbury, public domain

74HC138:

3-to-8 Line Decoder/Demultiplexer

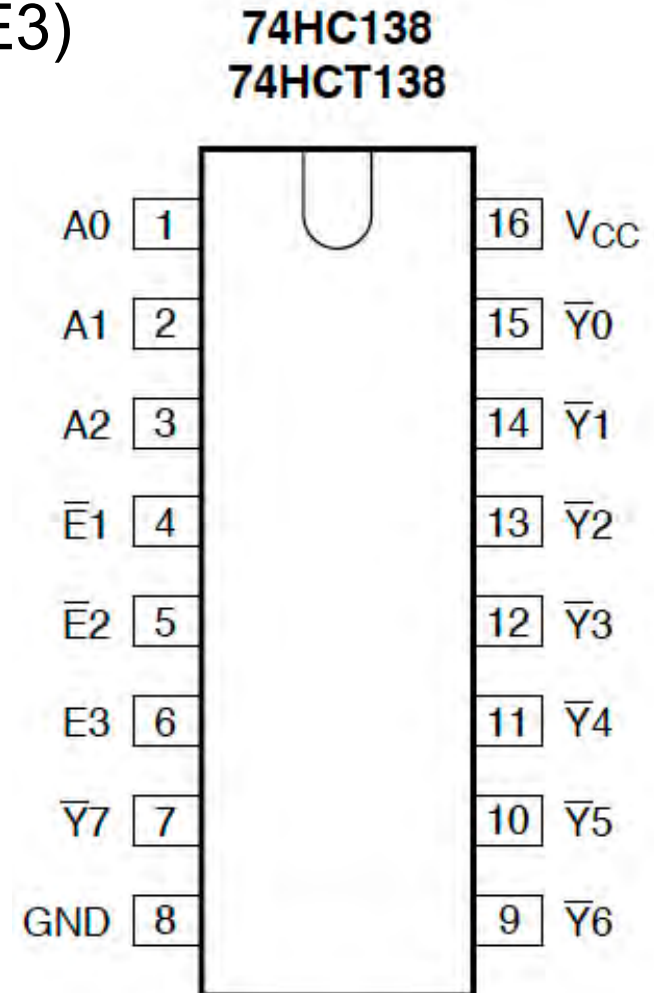
- Input $x = (\text{not}(E1) \text{ and } \text{not}(E2) \text{ and } E3)$
- Address lines $A0, A1, A2$ to select output $Y_{A0, A1, A2}$
- Output $Y_{A0, A1, A2} = \text{not}(x)$
- other outputs: $Y_i = 1$
- $V_{CC} = 5V$
- $I_{OUT} = \pm 25\text{mA}$



Source: Philips Datasheet

74HC154: 4-to-16 Line Decoder/Demultiplexer

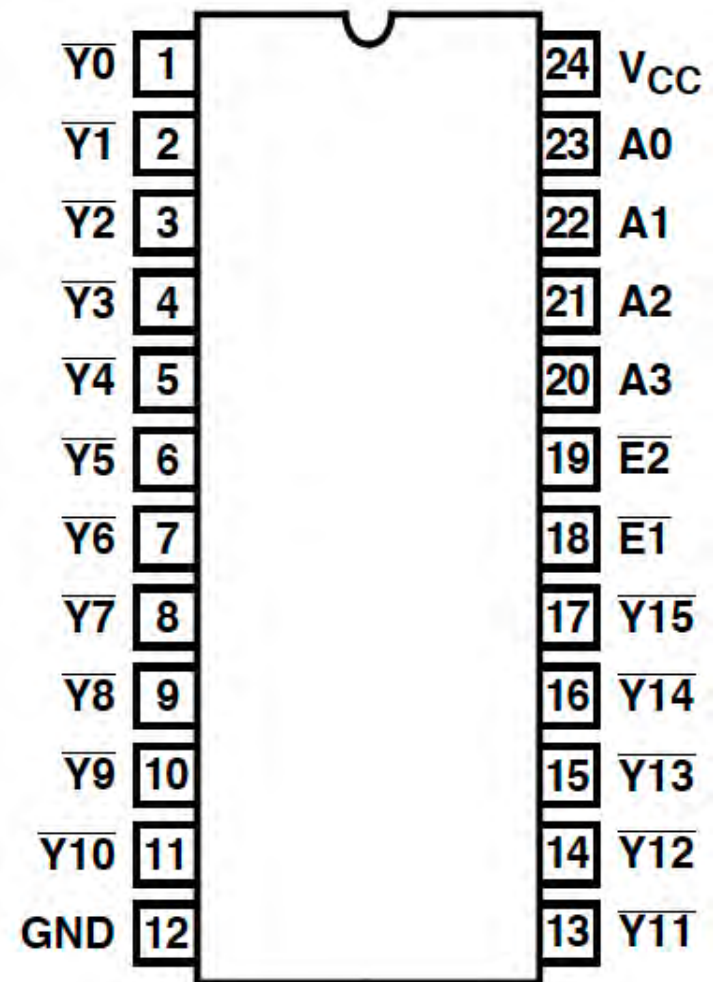- Input $x = (E1 \text{ or } E2)$
- Address lines $A0, A1, A2$ to select output $Y_{A0, A1, A2}$
- Output $Y_{A0, A1, A2} = x$
- other outputs: $Y_i = 1$
- $V_{CC} = 5V$
- $I_{OUT} = \pm 50mA$



Source: Harris Semiconductor Datasheet